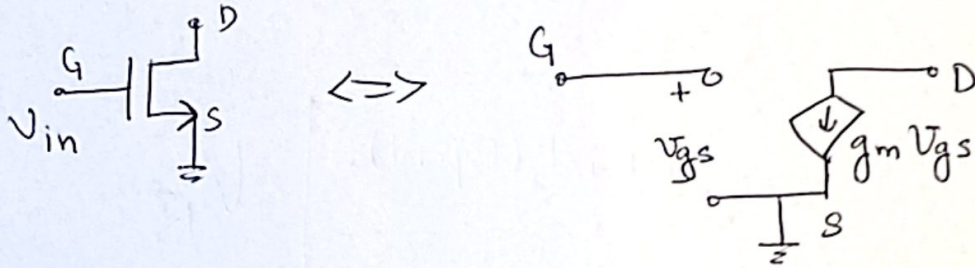



MOS Amplifiers [Low freq models]

> We want to amplify from V_{in} to V_{out} .



> To convert from current to voltage we place a load.

Common Source

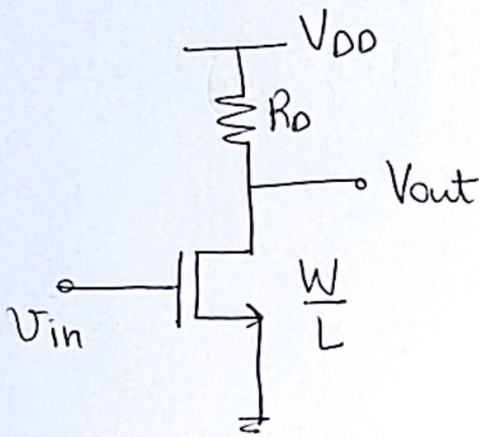

Saturation


$$V_{out} = V_{DD} - I_D R_D$$

$$= V_{DD} - R_D \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$


$$V_{out} = V_{DD} - R_D \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_T)^2 \right]$$

Triode
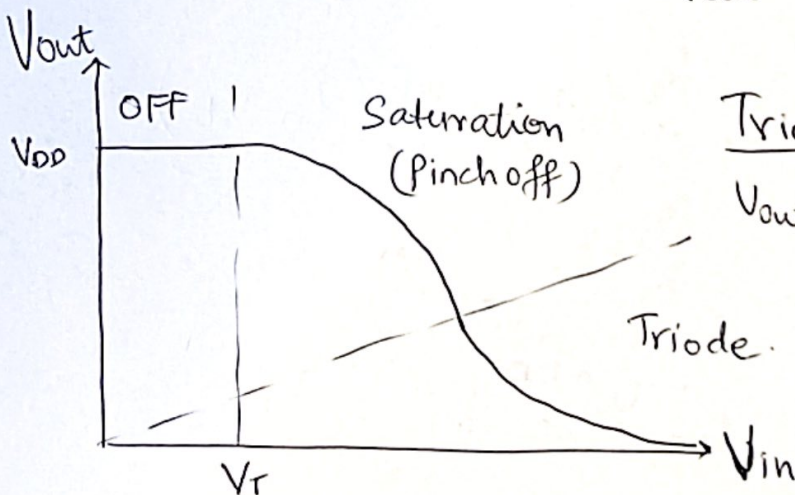
$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[(V_{in} - V_T) V_{out} - V_{out}^2 \right]$$



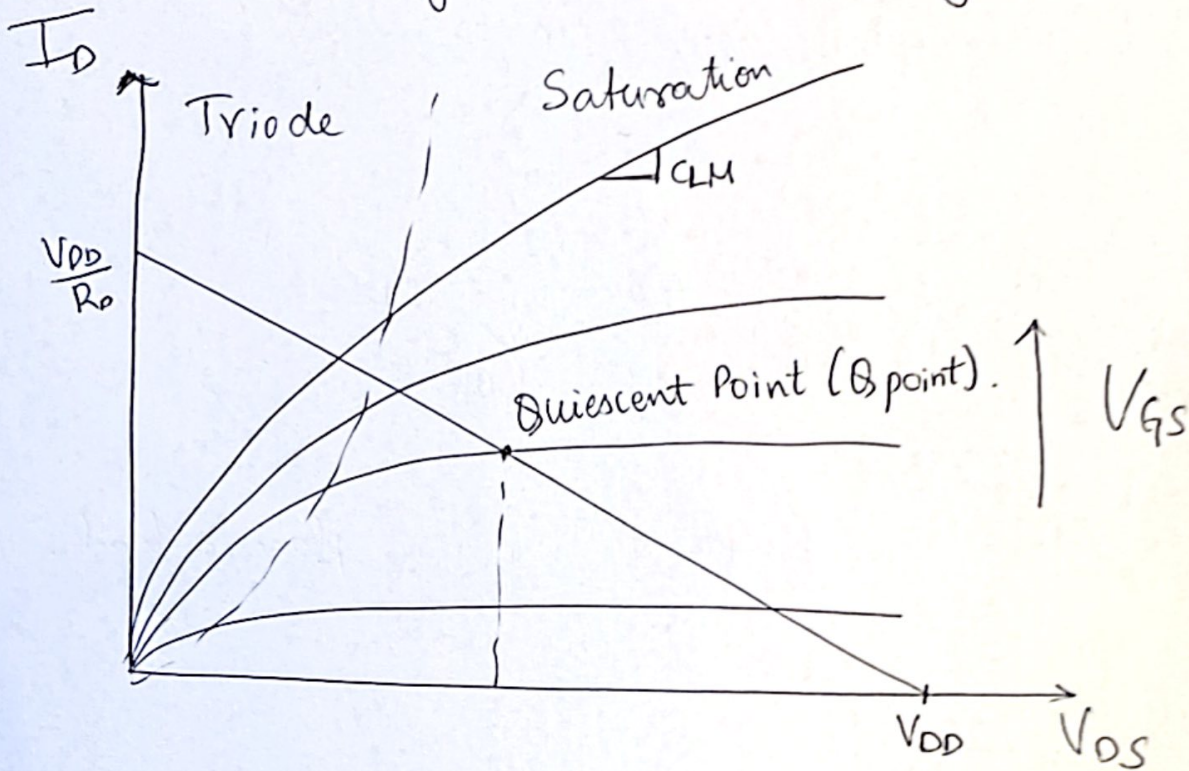load line analysis (Understanding Bias Points)




$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$V_{DS} = V_{DD} - I_D R_D$$

Small-Signal Gain

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = \frac{V_{out}}{V_{in}} = -R_D \underbrace{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_T)}_{g_m}$$

$$\boxed{A_v = -g_m R_D}$$

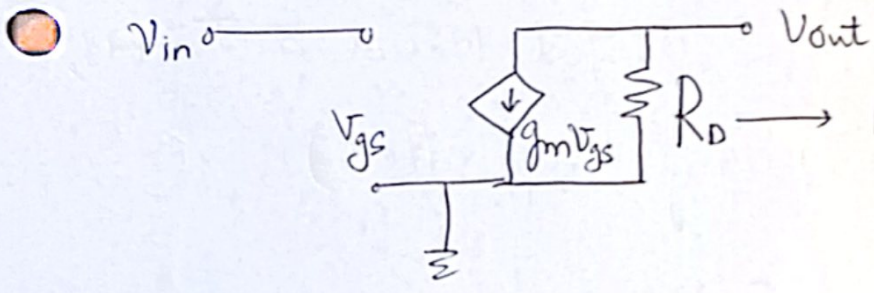

Note: V_{DD} becomes a Small Signal ground.

$$\Rightarrow V_{out} = -g_m V_{gs} R_D$$


$$\Rightarrow \boxed{A_v = -g_m R_D}$$

What about CLM?

$$V_{out} = V_{DD} - R_D \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_T)^2 (1 + \lambda V_{out}) \right]$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -\frac{\partial}{\partial V_{in}} \left(R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_T)^2 (1 + \lambda V_{out}) \right) \dots$$



too complex!

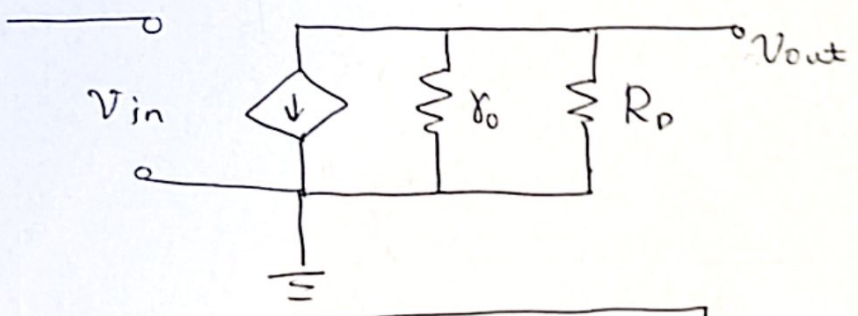

$$\Rightarrow \boxed{A_v = -g_m (R_D \parallel r_o)}$$



> Small Signal T-model (with body effect)
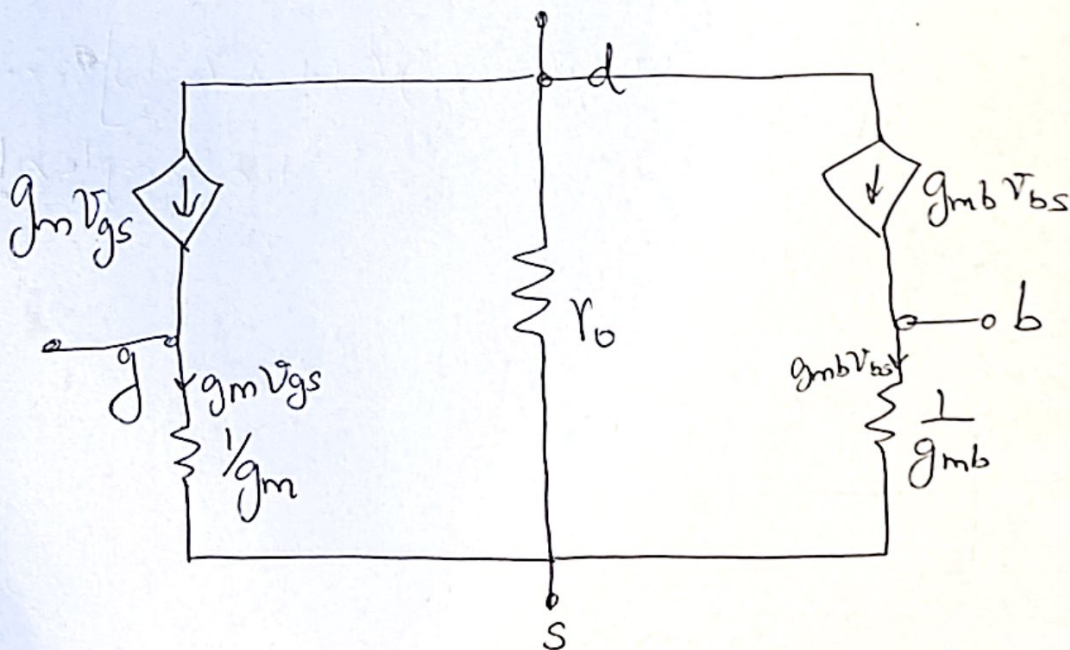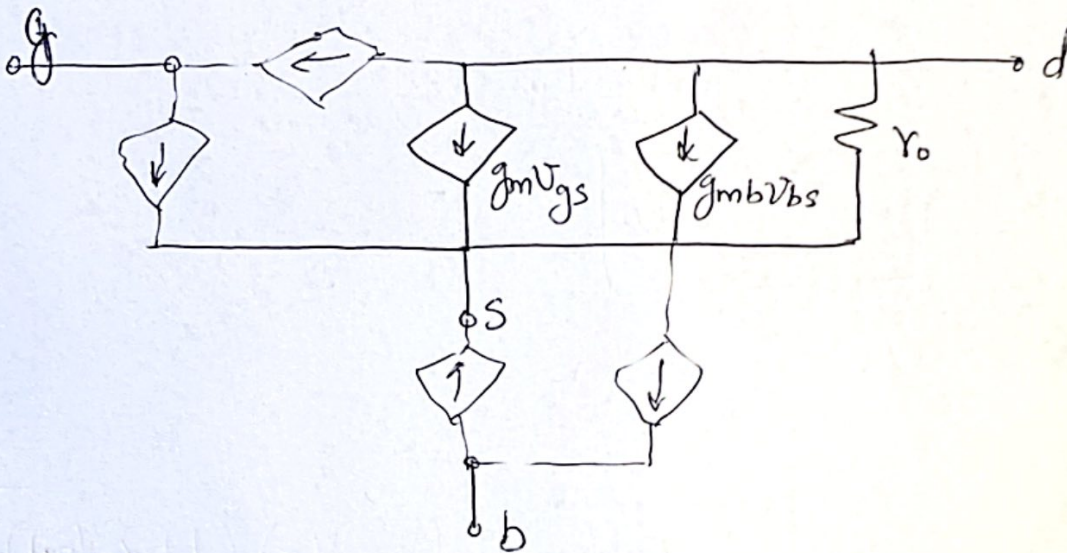
> Sometimes it is more useful to use a T-model, (especially when considering body effect)



> This shows explicitly the two back to back "transistors".

Source Degeneration

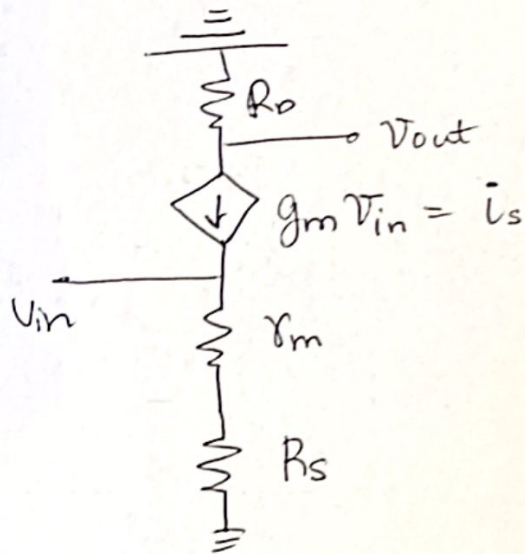
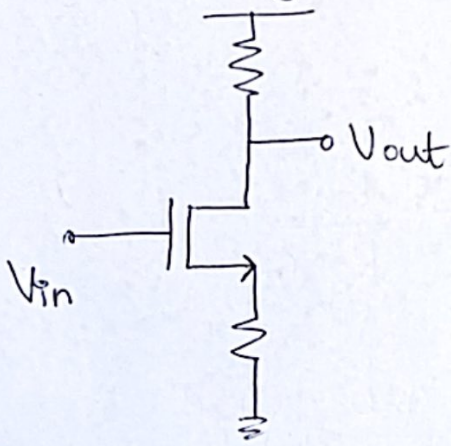


$$i_s = \frac{V_{in}}{R_s + r_m}$$

$$V_{out} = -i_s R_o$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = - \frac{R_o}{R_s + r_m} = - \frac{g_m R_o}{1 + g_m R_s}$$

What about body effect?

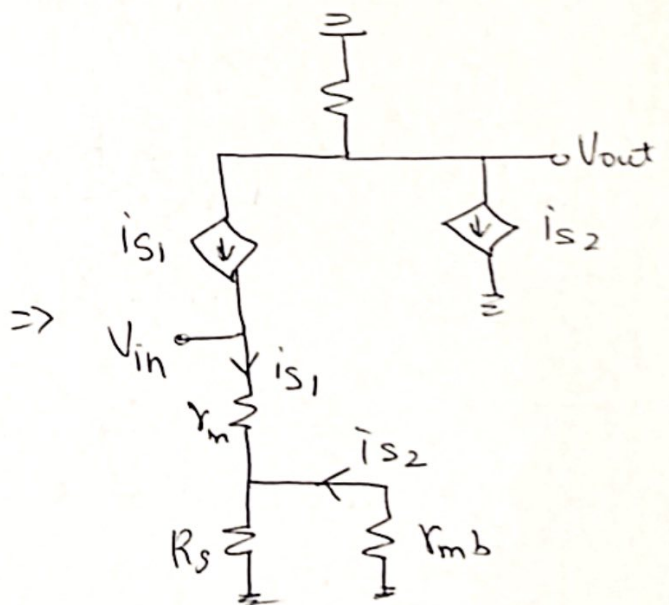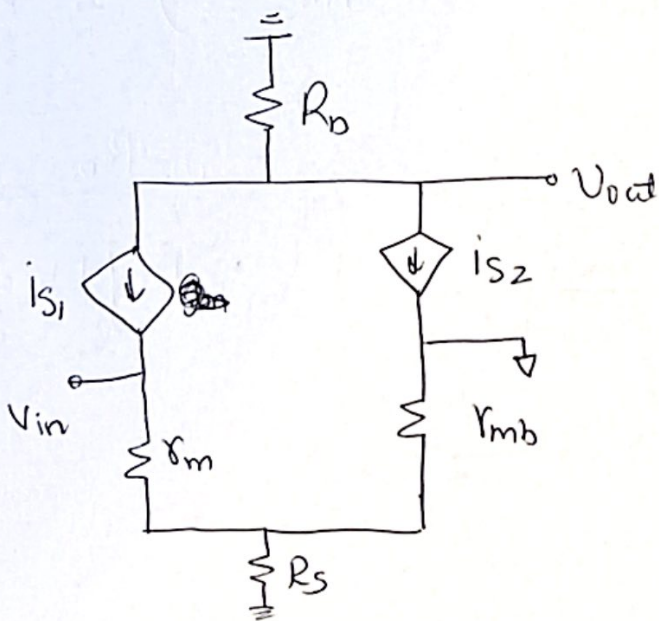

$$V_{out} = - \underbrace{(i_{s1} + i_{s2})}_{i_s} R_D$$

$$-i_{s2} = +i_{s1} \frac{R_s}{R_s + r_{mb}} \Rightarrow \bar{i}_s = \bar{i}_{s1} - i_{s1} \frac{R_s}{R_s + r_{mb}}$$

$$= i_{s1} \left(\frac{r_{mb}}{R_s + r_{mb}} \right)$$

Also,
$$i_{s1} = \frac{V_{in}}{r_m + (R_s \parallel r_{mb})} = V_{in} \frac{R_s + r_{mb}}{R_s r_m + R_s r_{mb} + r_m r_{mb}}$$

$$\Rightarrow V_{out} = -i_s R_D = -i_{s1} \left(\frac{r_{mb}}{R_s + r_{mb}} \right) R_D$$


$$\Rightarrow A_v = - \left(\frac{\cancel{R_s + r_{mb}}}{R_s r_m + R_s r_{mb} + r_m r_{mb}} \cdot \frac{r_{mb}}{\cancel{R_s + r_{mb}}} \cdot R_D \right)$$

$A_v = - \frac{R_D}{r_m + R_s \left(1 + \frac{r_m}{r_{mb}} \right)}$	$= \frac{-g_m R_D}{1 + g_m R_s \left(1 + \frac{r_{mb}}{g_m} \right)}$
-----------------------------------------------------------------------	------------------------------------------------------------------------


Diode Connected loads

> To avoid resistors.

> Always in *off* or pinch-off.

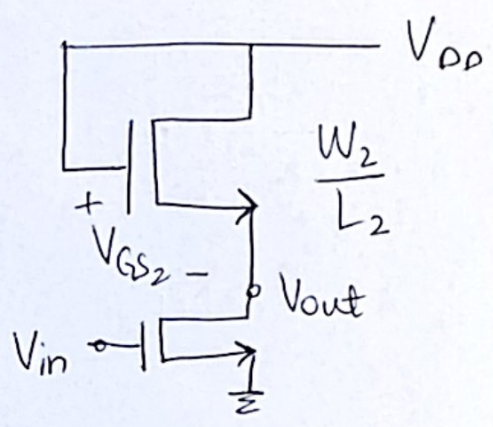
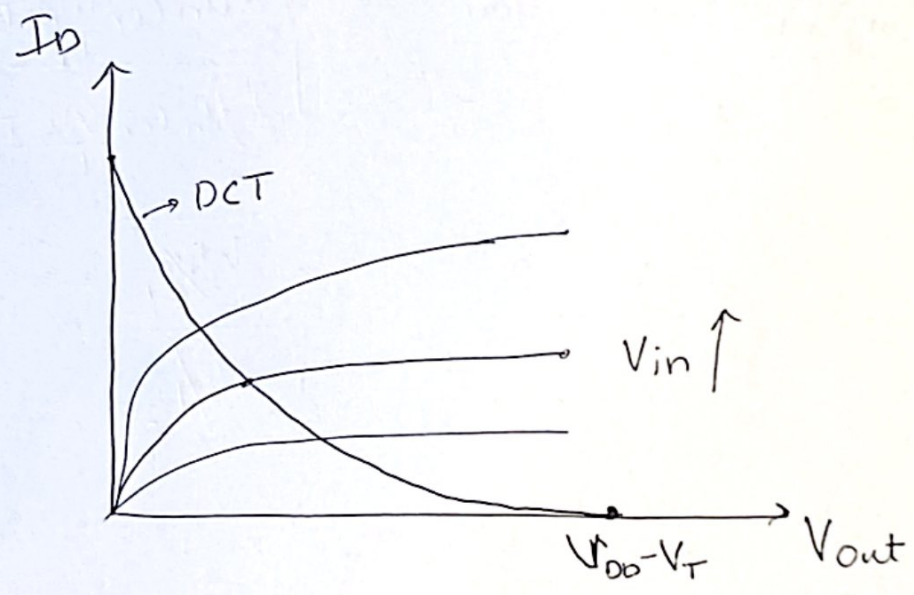
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} (V_{DD} - V_{out} - V_{T2})^2 = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{in} - V_{T1})^2$$




$$V_{out} = V_{DD} - V_{T2} - \sqrt{\frac{W_1/L_1}{W_2/L_2}} (V_{in} - V_{T1}) \rightarrow \text{Large signal Gain is "now" "Linear"}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = - \sqrt{\frac{W_1/L_1}{W_2/L_2}} \quad (\text{ignoring CLM})$$

→ Low distortion, well defined.

Small signal model

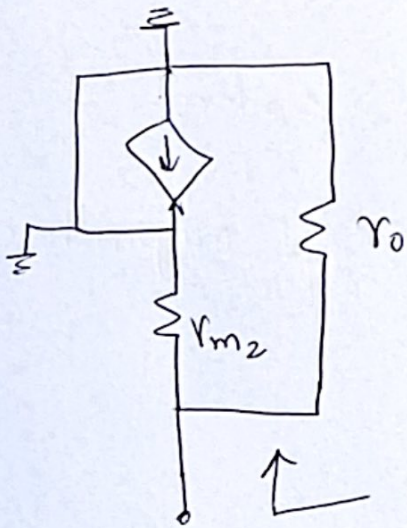

$$\begin{aligned} \Rightarrow A_v &= -g_{m1} r_{m2} = -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{2\mu_n C_{ox} \frac{W_1}{L_1} I_D}{2\mu_n C_{ox} \frac{W_2}{L_2} I_D}} \\ &= -\sqrt{\frac{W_1/L_1}{W_2/L_2}} \end{aligned}$$